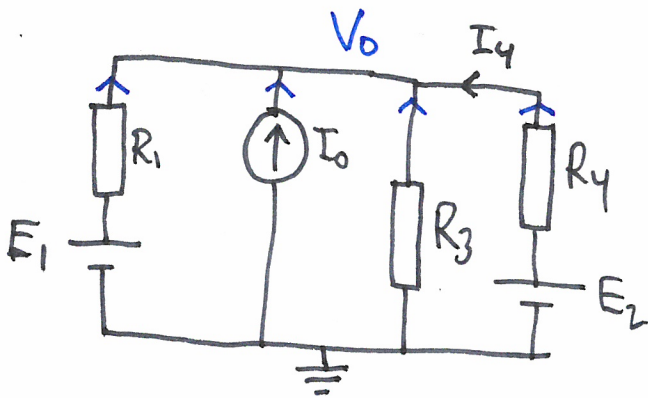


A 1.10) Lösning med hjälp av nodanalys:

Borttagning av  $R_2$  och eliminerig av  $E_1$  <sup>som ensam källa</sup> ~~ger~~:



$$E_1 = 1,5 \text{ V}, E_2 = 12 \text{ V}, I_0 = 1,5 \text{ A}$$

$$R_1 = 3,0 \, \Omega, R_2 = 7,0 \, \Omega$$

$$R_3 = 6,0 \, \Omega, R_4 = 2,0 \, \Omega$$

$$\frac{E_1 - V_0}{R_1} + I_0 + \frac{0 - V_0}{R_3} + \frac{E_2 - V_0}{R_4} = 0 \Rightarrow$$

$$\frac{E_1}{R_1} - \frac{V_0}{R_1} - \frac{V_0}{R_3} + \frac{E_2}{R_4} - \frac{V_0}{R_4} = -I_0 \Rightarrow$$

$$-\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4}\right) \cdot V_0 = -\frac{E_1}{R_1} - \frac{E_2}{R_4} - I_0 \Rightarrow$$

$$V_0 = \frac{-\frac{E_1}{R_1} - I_0 - \frac{E_2}{R_4}}{-\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4}\right)} = \frac{\frac{1,5}{3} + 1,5 + \frac{12}{2}}{\frac{1}{3} + \frac{1}{6} + \frac{1}{2}} = 8 \text{ V}$$

$$I_4 = \frac{E_2 - V_0}{R_4} = \frac{12 - 8}{2} = 2,0 \text{ A}$$

$$\boxed{I_4 = 2,0 \text{ A}}$$