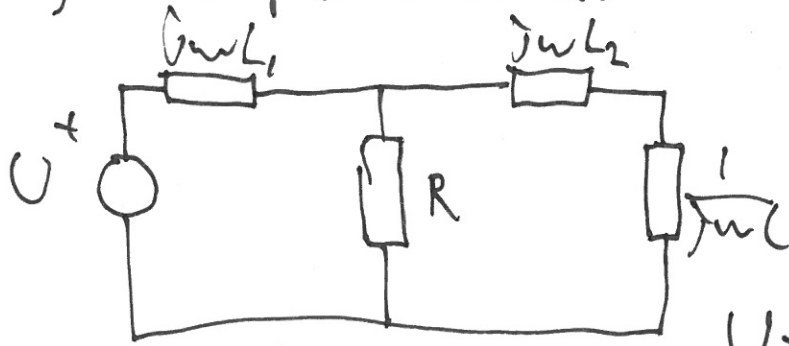


B 2.2) Komplexschema:



$$R = 3.0 \Omega$$

$$\omega L_1 = 2.0 \Omega$$

$$\omega L_2 = 2.0 \Omega$$

$$\frac{1}{\omega C} = 1.0 \Omega$$

$$U = 4.0 \cdot \sqrt{2}$$

$$Z_{\text{tot}} = j\omega L_1 + R \parallel (j\omega L_2 + \frac{1}{j\omega C})$$

$$= j\omega L_1 + \frac{R \cdot (j\omega L_2 + \frac{1}{j\omega C})}{R + j\omega L_2 + \frac{1}{j\omega C}}$$

$$= j \cdot 2 + \frac{3 \cdot (j \cdot 2 - j \cdot 1)}{3 + j \cdot 2 - j \cdot 1} = j \cdot 2 + \frac{j \cdot 3}{3 + j}$$

$$= j \cdot 2 + \frac{j \cdot 3 \cdot (3 - j)}{(3 + j)(3 - j)} = j \cdot 2 + \frac{j \cdot 9 + 3}{9 + 1} = j \cdot 2 + j \cdot 0.9 + 0.3$$

$$= 0.3 + j \cdot 2.9 \approx 2.92 \cdot e^{j \cdot 1.47} \Omega$$

$$I = \frac{U}{Z_{\text{tot}}} = \frac{4 \cdot \sqrt{2}}{2.92 \cdot e^{j \cdot 1.47}} = \sqrt{2} \cdot \underbrace{1.37}_{I_e} \cdot e^{-j \cdot 1.47}$$

Scheinbar effekt:

$$S = U_e \cdot I_e = 4 \cdot 1.37 = 5.48 \text{ VA}$$

Aktiv effekt: 1.47

$$P = U_e I_e \cos \varphi = 4 \cdot 1.37 \cdot \cos(1.47) = 0.56 \text{ W}$$

Reaktiv effekt:

$$Q = U_e I_e \sin \varphi = 5.45 \text{ W}$$