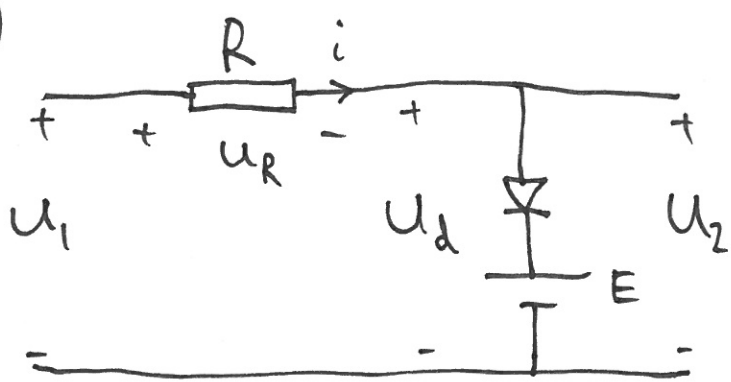



D1)



$R = 1.0 \text{ k}\Omega$   
 $E = 5.0 \text{ V}$

$i = 0 \Rightarrow u_D = u_1 \Rightarrow$

$u_1 < E \Rightarrow$  Dioden spärnar

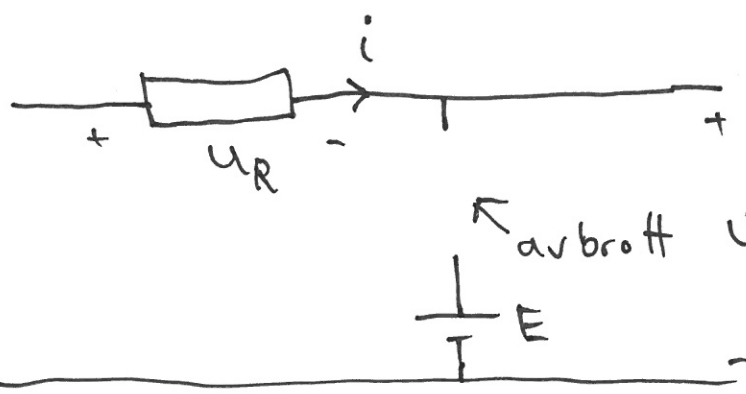

$i = 0 \Rightarrow u_R = 0$

↑ avbrött  $u_2 \Rightarrow u_2 = u_1$

$u_1 \leq E \Rightarrow$  Dioden leder

