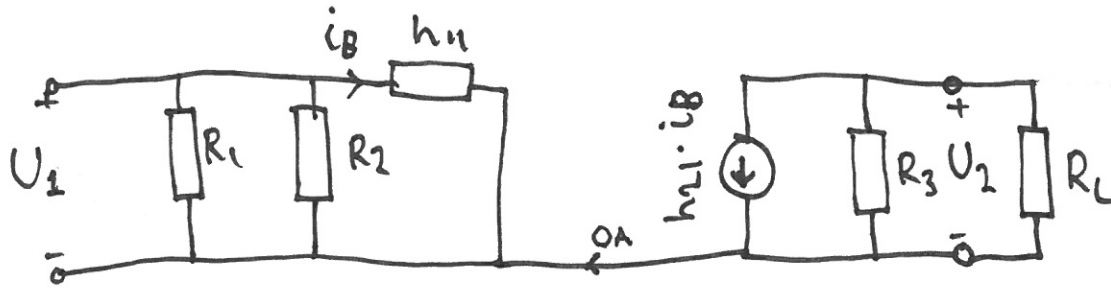


E-12) Småsignalschema



$R_1 = 40 \text{ k}\Omega$
 $R_2 = 20 \text{ k}\Omega$
 $R_3 = 4,0 \text{ k}\Omega$
 $R_4 = 1,0 \text{ k}\Omega$
 $R_L = 6,0 \text{ k}\Omega$

$$F = \frac{U_2}{U_1} = \frac{-h_{21} \cdot i_B \cdot \frac{R_3 \cdot R_L}{R_3 + R_L}}{h_{11} \cdot i_B} = \frac{-h_{21}}{h_{11}} \cdot \frac{R_3 \cdot R_L}{R_3 + R_L}$$

$h_{11} = 500 \Omega$
 $h_{12} \approx 0$
 $h_{21} = 39$
 $h_{22} \approx 0$

$$= \frac{-39}{500} \cdot \frac{4 \text{ k} \cdot 6 \text{ k}}{4 \text{ k} + 6 \text{ k}} = -1,87$$

$F = -1,87$


$$Z_{in} = R_1 \parallel R_2 \parallel h_{11} = \frac{R_1 \cdot R_2 \cdot h_{11}}{R_1 \cdot R_2 + R_1 \cdot h_{11} + R_2 \cdot h_{11}} = 482 \Omega$$

$Z'_{in} = 482 \Omega$

$$Z_{ut} = R_3 = 4,0 \text{ k}\Omega$$

$Z_{ut} = 4,0 \text{ k}\Omega$

Utän emitter ankoppling:

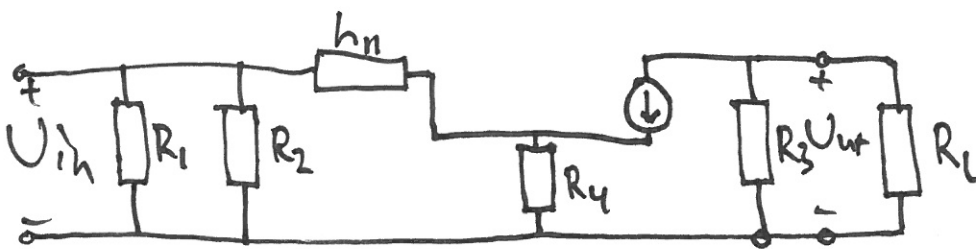

$$F = \frac{U_{ut}}{U_{1n}} = \frac{-h_{21} \cdot i_B \cdot \frac{R_3 \cdot R_L}{R_3 + R_L}}{i_B \cdot h_{11} + (i_B + h_{21} \cdot i_B) \cdot R_4} = \frac{-h_{21} \cdot \frac{R_3 \cdot R_L}{R_3 + R_L}}{h_{11} + (1 + h_{21}) \cdot R_4}$$

$$= \frac{-39 \cdot 2400}{500 + 40 \cdot 1000} = -2,31$$

$F = -2,31$