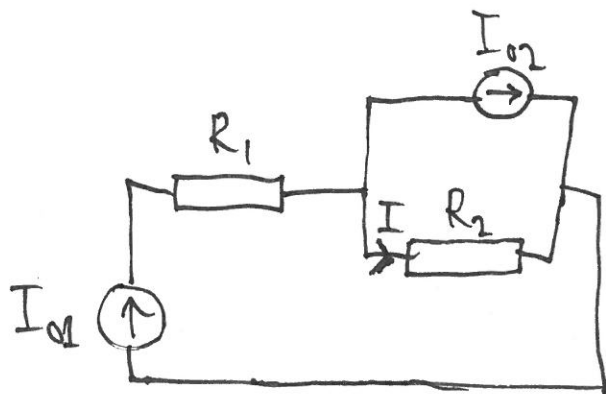


(-1)



$$I_{o1} = 10 \text{ mA}$$
$$I_{o2} = 5 \text{ mA}$$

KCL:

$$I + I_{o2} = I_{o1} \Leftrightarrow I = I_{o1} - I_{o2} = 10 \text{ mA} - 5 \text{ mA} = 5 \text{ mA}$$

$$I = 5 \text{ mA}$$