

2-14

Given spänning på komplex form:

$$U = 230 \cdot \sqrt{2} \cdot e^{j \cdot 0} = 230 \cdot \sqrt{2}$$


$$R = 10^3 \Omega$$

$$L = 0.5 \text{ H}$$

$$C = 0.1 \mu\text{F}$$


Komplex schema:

$$\omega = 2\pi \cdot 400$$

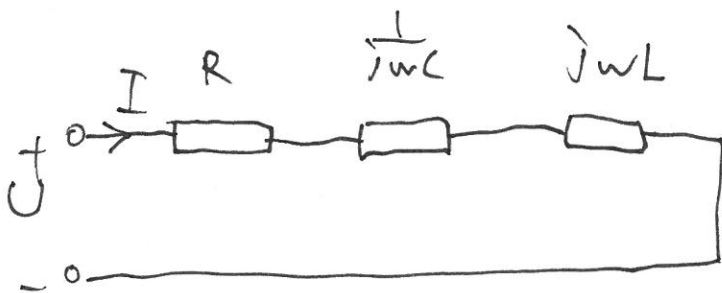

$$Z_{\text{tot}} = R + \frac{1}{j\omega C} + j\omega L$$
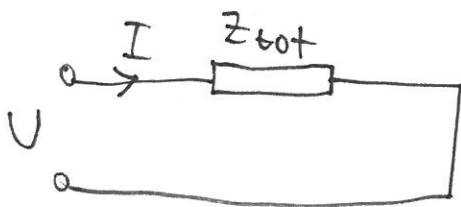
$$= 10^3 + \frac{1}{j \cdot 2\pi \cdot 400 \cdot 0.1 \cdot 10^{-6}} + j \cdot 2\pi \cdot 400 \cdot 0.5$$



$$= 10^3 + \frac{1}{j} \cdot \frac{1}{\pi \cdot 8 \cdot 10^{-5}} + j \cdot \pi \cdot 400$$

$$= 10^3 + j \cdot \left(\pi \cdot 400 - \frac{1}{\pi \cdot 8 \cdot 10^{-5}} \right)$$

$$= 10^3 + j \cdot 2722 = 2900 \cdot e^{-j \cdot 1.219}$$

$$I = \frac{U}{Z_{\text{tot}}} = \frac{230 \cdot \sqrt{2}}{2900 \cdot e^{-j \cdot 1.219}} = 0.112 \cdot e^{j \cdot 1.219}$$



$$i(t) = 0.112 \cdot \sin(2\pi \cdot 400 \cdot t + 1.219) \text{ A}$$

$$i(t) = 0.112 \cdot \sin(2\pi \cdot 400 \cdot t + 1.219) \text{ A}$$