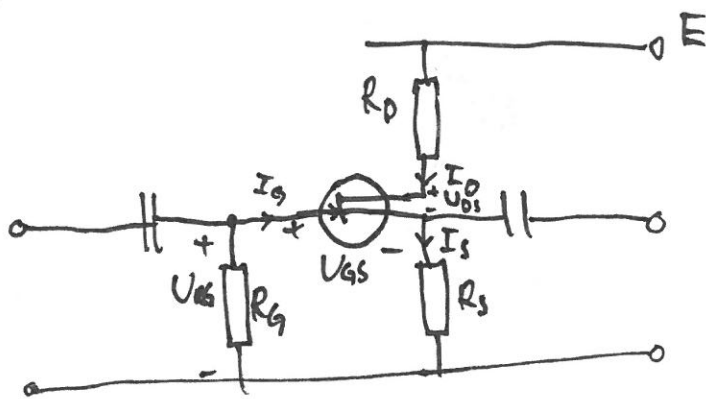


3-24)



$$I_D = 2 \text{ mA}$$

$$R_S = 1 \text{ k}\Omega$$

$$R_D = 4 \text{ k}\Omega$$

$$I_G \approx 0 \Rightarrow U_{RG} \approx 0, I_S = I_D$$

KVL:

$$1: U_{RG} - U_{GS} - I_D \cdot R_S \Leftrightarrow U_{GS} = -I_D \cdot R_S = -2 \text{ mA} \cdot 1 \text{ k} = -2 \text{ V}$$

$$2: -I_D \cdot R_S + E - I_D \cdot R_D - U_{DS} = 0$$

$$\Rightarrow U_{DS} = E - I_D \cdot (R_S + R_D) = 30 - 2 \text{ mA} \cdot 5 \text{ k} = 20 \text{ V}$$

| |
|---|
| $U_{GS} = -2 \text{ V}$ $U_{DS} = 20 \text{ V}$ |
|---|