


4-3) Likströmschema:

$$E = 10V, R_C = 2k\Omega$$

$$B = 100, U_{BEQ} = 0.7V$$

$$I_{CQ} = 3.5mA, U_{CEQ} = 4.5V$$

$$R_1 // R_2 = 0.1 \cdot B \cdot R_E$$

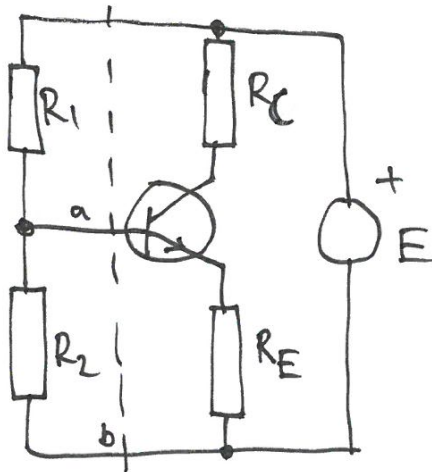

$$R_E = \frac{U_{RE}}{I_E} = \frac{E - R_C I_{CQ} - U_{CEQ}}{I_C \cdot (1 + \frac{1}{B})} = \frac{2.0}{3.535m} = 565.8\Omega$$

Bestäm  $R_1$  &  $R_2$ :

$$R_{ab} = R_1 // R_2 = 0.1 \cdot B \cdot R_E = 5.658k\Omega$$

$$U = \frac{E \cdot R_2}{R_1 + R_2} \Rightarrow \frac{U}{E} = \frac{R_2}{R_1 + R_2} (*)$$

KVL:

$$U - I_b \cdot R_{ab} - U_{BEQ} - U_{RE} = 0 \Leftrightarrow$$

$$U = I_{CQ} / B \cdot R_{ab} + U_{BEQ} + U_{RE} = 3.5m / 100 \cdot 5.658k + 0.7 + 2 = 2.898V$$

$$R_{ab} = R_1 // R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2} \stackrel{(*) \text{ insatt}}{=} \frac{R_1 \cdot U}{E} \Rightarrow R_1 = \frac{R_{ab} \cdot E}{U} = 19.52k\Omega$$

$$R_{ab} = \frac{R_1 \cdot R_2}{R_1 + R_2} \Rightarrow R_2 = \frac{R_{ab} \cdot R_1}{R_1 - R_{ab}} = 7.97k\Omega$$

Se även boken s. (332) 336-337!

|                     |
|---------------------|
| $R_E = 567\Omega$   |
| $R_1 = 19.5k\Omega$ |
| $R_2 = 7.97k\Omega$ |

