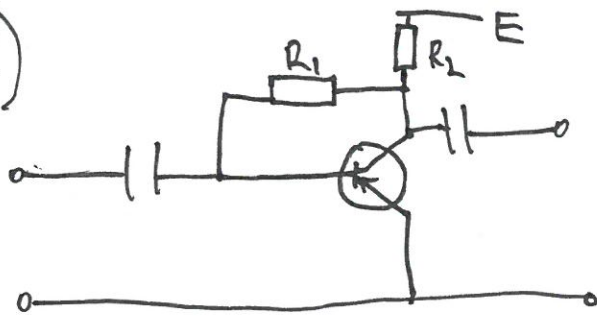


4-4)



$$E = -1,3 \text{ V}$$


$$B = 50$$

$$R_1 = 1,2 \text{ M}\Omega$$

$$R_2 = 3,3 \text{ k}\Omega$$

$$U_{BE} = -0,1 \text{ V}$$

Likströmsschema:

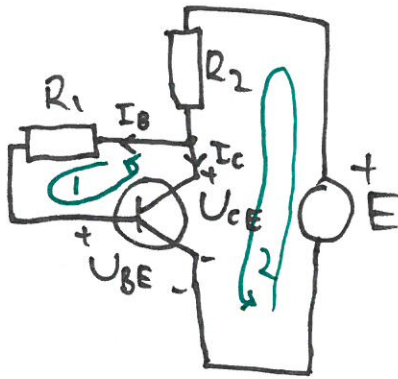

$$1: -U_{BE} + U_{CE} - I_B \cdot R_1 = 0 \quad (1)$$

$$2: E - (I_C + I_B) \cdot R_2 - U_{CE} = 0 \quad (2)$$

$$I_C = B \cdot I_B \quad (3)$$

(2) o (3) insatta i (1) ger:

$$-U_{BE} + E - (B \cdot I_B + I_B) \cdot R_2 - I_B \cdot R_1 = 0 \Leftrightarrow$$

$$E - U_{BE} = (B + 1) \cdot R_2 + R_1 \cdot I_B \Leftrightarrow$$

$$I_B = \frac{E - U_{BE}}{R_1 + (B + 1) \cdot R_2} = \frac{-1,3 - -0,1}{1,2 \text{ M} + 51 \cdot 3,3 \text{ k}} \approx -0,877 \mu\text{A}$$

$$(3) \Rightarrow I_C \approx -43,9 \mu\text{A}$$

$$(2) \Rightarrow U_{CE} = E - R_2 (I_C + I_B) \approx -1,15 \text{ V}$$

$$I_{BQ} = -0,877 \mu\text{A}$$

$$I_{CQ} = -43,9 \mu\text{A}$$

$$U_{CEQ} = -1,15 \text{ V}$$