

10.1) Lösning:
Sanningstabell:

Q_A	Q_B	Q_C	J_A	K_A	J_B	K_B	J_C	K_C	Q_A^+	Q_B^+	Q_C^+
0	0	0	0	0	1	0	0	0	0	1	0
0	0	1	0	0	0	0	0	1	0	0	0
0	1	0	1	0	0	1	1	0	1	0	1
0	1	1	1	0	0	0	0	1	1	1	0
1	0	0	0	1	1	0	1	0	0	1	1
1	0	1	0	0	0	0	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0	0	1
1	1	1	0	0	0	0	0	1	1	1	0

Tillståndsdigram:

