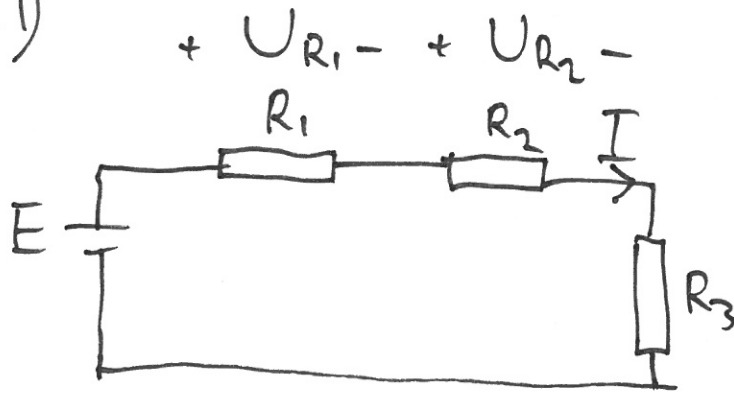


A 2.1)



$$I = 5 \text{ A}$$

$$R_3 = 2 \Omega$$

$$P_{R_2} = 25 \text{ W}$$

$$U_{R_1} = 20 \text{ V}$$

$$E = R_{\text{tot}} \cdot I$$

$$R_{\text{tot}} = R_1 + R_2 + R_3$$

R_1 ?

$$U_{R_1} = R_1 \cdot I \Rightarrow R_1 = \frac{U_{R_1}}{I} = \frac{20}{5} = 4 \Omega$$

R_2 ?

$$P_{R_2} = U_{R_2} \cdot I \Rightarrow U_{R_2} = \frac{P_{R_2}}{I} = \frac{25}{5} = 5 \text{ V}$$

$$U_{R_2} = R_2 \cdot I \Rightarrow R_2 = \frac{U_{R_2}}{I} = \frac{5}{5} = 1 \Omega$$

$$R_{\text{tot}} = 4 + 1 + 2 = 7 \Omega$$

$$E = 7 \cdot 5 = 35 \text{ V}$$

$$\boxed{E = 35 \text{ V}}$$