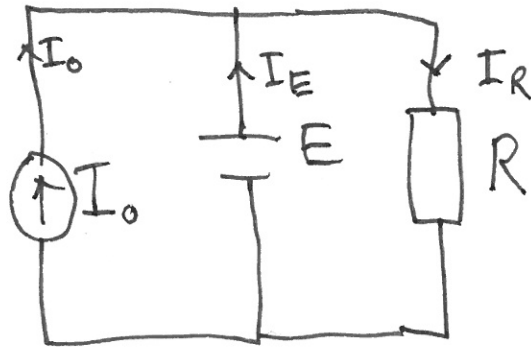


A.2.3)



$$I_0 = 0.4 \text{ A}$$

$$E = 10 \text{ V}$$

$$R = 20 \Omega$$

KCL:

$$I_R = I_0 + I_E \Leftrightarrow I_E = I_R - I_0 \quad (1)$$

Ohm's law:

$$E = R \cdot I_R \Rightarrow I_R = \frac{E}{R} = \frac{10}{20} = 0.5 \text{ A}$$

$$P_{\text{tot}} = I_R \cdot E = 0.5 \cdot 10 = 5 \text{ W}$$

$$P_{I_0} = I_0 \cdot E = 0.4 \cdot 10 = 4 \text{ W}$$

$$(1) \Rightarrow I_E = 0.5 - 0.4 = 0.1 \text{ A}$$

$$P_E = I_E \cdot E = 0.1 \cdot 10 = 1 \text{ W}$$

$P_{I_0} = 4 \text{ W}$
$P_E = 1 \text{ W}$