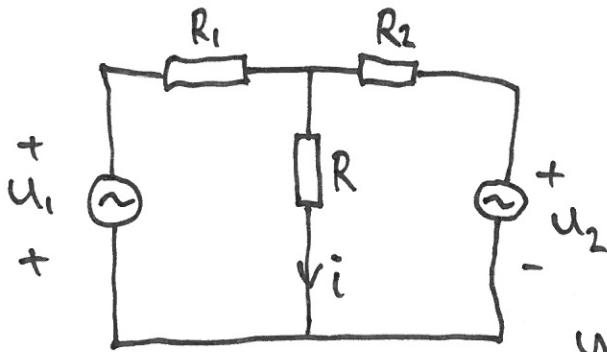


B 1.10)

$$u_1(t) = 30\sqrt{2} \cdot \sin(\omega \cdot t) \text{ V}$$



$$R_1 = 1.0 \text{ k}\Omega$$

$$R_2 = 1.0 \text{ k}\Omega$$


$$R = 1.0 \text{ k}\Omega$$

$$u_2(t) = 60 \cdot \sin(\omega \cdot t + 45^\circ) \text{ V}$$

Beräkna i med superpositionen:

Nollställ U_1 och beräkna I' :

Komplex schema:

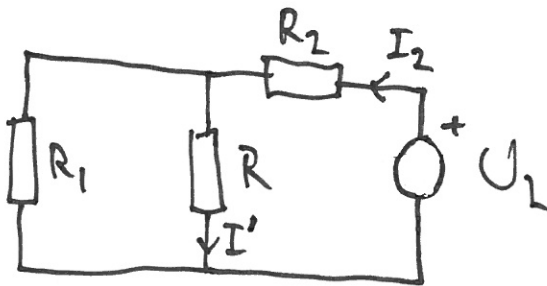

$$U_2 = 60 \cdot e^{j \cdot \pi/4} \text{ V}$$


$$R_{\text{tot}} = R_2 + R_1 \parallel R = 1 \text{ k} + \frac{1 \text{ k} \cdot 1 \text{ k}}{1 \text{ k} + 1 \text{ k}} = 1.5 \text{ k } \Omega$$

$$I_2 = \frac{U_2}{R_{\text{tot}}} = \frac{60 \cdot e^{j \cdot \pi/4}}{1.5 \text{ k}} = 40 \text{ m} \cdot e^{j \cdot \pi/4} \text{ A}$$

Strömdelning:

$$I' = \frac{I_2 \cdot R_1}{R_1 + R} = \frac{40 \text{ m} \cdot e^{j \cdot \pi/4} \cdot 1 \text{ k}}{2 \text{ k}} = 20 \text{ m} \cdot e^{j \cdot \pi/4} \text{ A}$$

Nollställ u_2 och beräkna i'' :

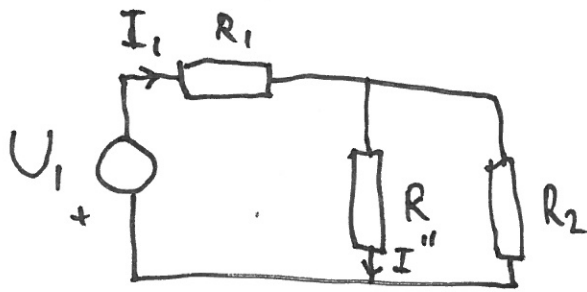

$$U_1 = 30 \cdot \sqrt{2} \cdot e^{j \cdot 0} \text{ V}$$

$$I_1 = -U_1 / (R_1 + R // R_2) = \frac{-30 \cdot \sqrt{2}}{1.5 \text{ k}} = -20\sqrt{2} \text{ mA}$$

Strömdelning:

$$I'' = \frac{I_1 \cdot R_2}{R + R_2} = \frac{-20\sqrt{2} \text{ mA} \cdot 1 \text{ k}}{2 \text{ k}} = -10\sqrt{2} \text{ mA}$$

$$\begin{aligned} I &= I' + I'' = 20 \text{ mA} \cdot e^{j\pi/4} - 10\sqrt{2} \text{ mA} = \\ &= 20 \text{ mA} (\cos \frac{\pi}{4} + j \cdot \sin \frac{\pi}{4}) - 10\sqrt{2} \text{ mA} = \\ &= 20 \text{ mA} \cdot \left(\frac{\sqrt{2}}{2} + j \cdot \frac{\sqrt{2}}{2} \right) - 10\sqrt{2} \text{ mA} = \\ &= 10\sqrt{2} \text{ mA} + j \cdot 10\sqrt{2} \text{ mA} - 10\sqrt{2} \text{ mA} = j \cdot 10\sqrt{2} \text{ mA} \\ &= 10\sqrt{2} \cdot e^{j\pi/2} \text{ mA} \end{aligned}$$

$$\Rightarrow i(t) = 10\sqrt{2} \cdot \sin(\omega t + \pi/2) \text{ mA}$$