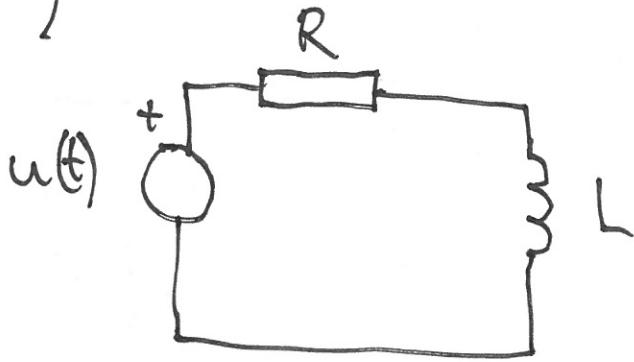


C-2)




$$R = 10 \Omega$$

$$L = 0.20 \text{ H}$$

$$u(t) = 50 \cdot e^{-100t} \text{ V}$$

⇓ operatorschema

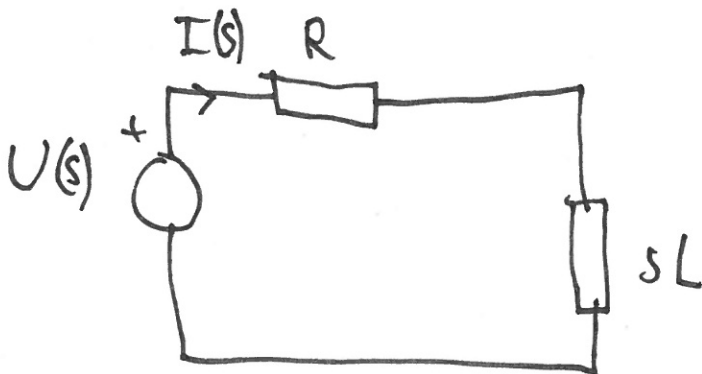

$$I(s) = \frac{U(s)}{R + sL}$$

$$\text{Parlösen} \Rightarrow U(s) = 50 \cdot \frac{1}{s + 100}$$

$$\Rightarrow I(s) = \frac{\frac{50}{s + 100}}{10 + 0.2s} = \frac{1}{s + 100} \cdot 50 \cdot \frac{1}{10 + 0.2s} = 250 \cdot \frac{1}{s + 100} \cdot \frac{1}{s + 50}$$

$$\Rightarrow i(t) = \frac{A}{s + 100} + \frac{B}{s + 50} \quad (*), A = -5 \text{ och } B = 5$$

$$\Rightarrow i(t) = -5 \cdot e^{-100t} + 5 \cdot e^{-50t}$$