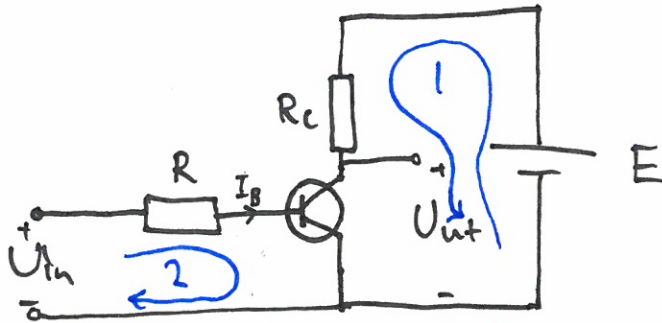


E-7)

Litströms schema:



$$E = 5.0 \text{ V}$$

$$R_c = 625 \Omega$$

$$h_{FE} = 50$$

$$U_{BE} = 0.7 \text{ V}$$

$$(1) \quad E - R_c \cdot I_c - U_{ut} = 0$$

Antag $U_{ut} = 0$ vid bootning

$$(1) \Rightarrow I_c = \frac{E}{R_c} = \frac{5}{625} = 8 \text{ mA}$$

$$\tilde{I}_B = \frac{I_c}{h_{FE}} = \frac{8 \text{ mA}}{50} = 160 \mu\text{A}$$

Basströmmen dubbelt så stor ger

$$I_B = 2 \cdot \tilde{I}_B = 320 \mu\text{A}$$

$$(2) \quad U_{in} - R \cdot I_B - U_{BE} = 0 \Rightarrow$$

$$R = \frac{U_{in} - U_{BE}}{I_B} = \frac{5 - 0.7}{320 \mu} = 13.4 \text{ k}\Omega$$

Transistorn bootnar för

$$R = 13.4 \text{ k}\Omega$$

redan $I_B = \tilde{I}_B$

$$(2) \Rightarrow U_{in} = U_{BE} + R \cdot \tilde{I}_B = 13.4 \text{ k} \cdot 160 \mu + 0.7 = 2.84 \text{ V}$$

$$U_{in} \geq 2.84 \text{ V}$$