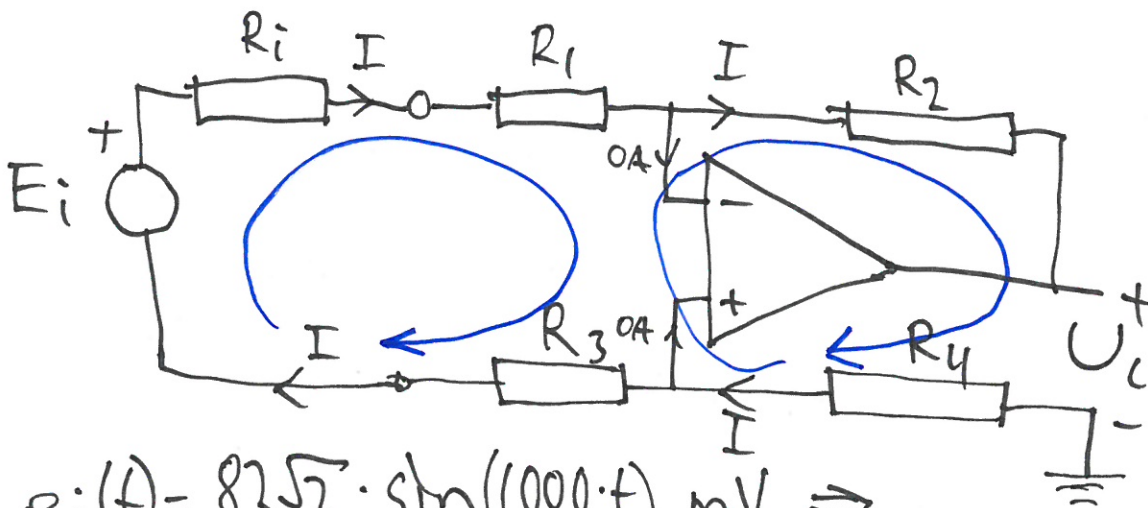


F 1-5) Lösung med "reell jw-analys":

(komplex)schema:



$$\begin{aligned} R_1 &= 12 \text{ k}\Omega \\ R_2 &= 270 \text{ k}\Omega \\ R_3 &= 12 \text{ k}\Omega \\ R_4 &= 270 \text{ k}\Omega \\ R_i &= 33 \text{ k}\Omega \end{aligned}$$

$$e_i(t) = 82\sqrt{2} \cdot \sin(1000 \cdot t) \text{ mV} \Rightarrow$$

$$E_i = 82 \cdot \sqrt{2} \text{ mV}$$

$$E_i - R_i \cdot I - R_1 \cdot I - R_3 \cdot I = 0 \quad (1)$$

$$-R_2 \cdot I - U_C - R_4 \cdot I = 0 \quad (2)$$

$$(1) \Rightarrow I = \frac{E_i}{R_i + R_1 + R_3}$$

$$(2) \Rightarrow U_C = -(R_2 + R_4) \cdot I$$

$$\begin{aligned} (1), (2) \Rightarrow U_C &= \frac{-(R_2 + R_4)}{R_i + R_1 + R_3} \cdot E_i = \frac{-(270 \text{ k} + 270 \text{ k})}{33 \text{ k} + 12 \text{ k} + 12 \text{ k}} \cdot 82\sqrt{2} \text{ m} = \\ &= \frac{-540 \text{ k}}{57 \text{ k}} \cdot 82\sqrt{2} \text{ m} = -0.78 \cdot \sqrt{2} \end{aligned}$$

\Rightarrow

$$u_C(t) = -0.78 \cdot \sqrt{2} \cdot \sin(1000t) \text{ V}$$