



LINKÖPING UNIVERSITY

Electrical interconnects revitalized

Christer Svensson
Linköping University

Christer Svensson, VLSI Design 2002

1



LINKÖPING UNIVERSITY

Electrical interconnects revitalized

Christer Svensson
Dept. of Electrical Engineering
Linköping University
58183 Linköping, Sweden
Phone: +46 13281223
Fax: +46 13139282
Email: chs@isy.liu.se

Christer Svensson, VLSI Design 2002


2

Outline

- Introduction
- Modeling transmission lines
- Step response
- Wire performance
- Wires in real systems
- Conclusion

Introduction

 Electrical interconnects are considered to be *the* major limitation to performance of scaled electronics.



Wire delay $\sim RC$

$$RC = \frac{\rho L}{t_m w} \frac{\epsilon w L}{t_i} = \rho \epsilon \frac{L^2}{t_m t_i}$$

Wire delay scales as (feature size)⁻²
Logic delay scales as (feature size)

Introduction

Some recent results indicates that this view may be wrong.

The objective of this lecture is to make us understand the *fundamental* limits of electrical interconnects and compare them to optical alternatives.

We want to demonstrate the *opportunities* offered by electrical interconnects.


Introduction

As we are looking for fundamental limits, we will use a *simplified view*: The transmission line view (assuming a well-behaved return path, e.g. a ground plane).

There are two motivations for this simplified view:

- It will give an upper limit to performance, which can be approached in practice.
- It will compare well with alternative solutions, which normally are not implemented and therefore also use simplified views.

Modeling transmission lines

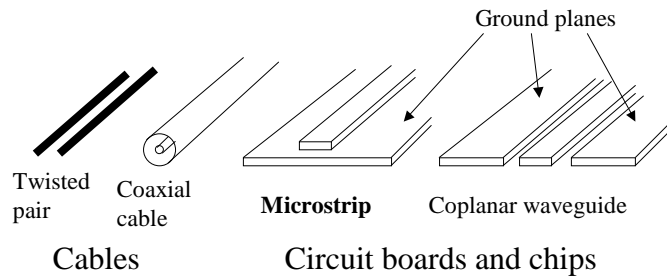


(Always a return path!)

We will concentrate on microstrip in the following

Modeling transmission lines

Circuit model:

 

z, y impedance och admittance per unit length

$$\frac{\partial v}{\partial x} = zi \quad \frac{\partial i}{\partial x} = yv \quad \Rightarrow \quad \frac{\partial^2 v}{\partial x^2} = zyv$$

General solution:

$$v = v(0)e^{\pm\sqrt{zy}x} \quad i = \frac{1}{z} \frac{\partial v}{\partial x} = \pm \sqrt{\frac{y}{z}} v = \frac{v}{Z_c}$$

Modeling transmission lines

Interpretation for a lossless line:

$$z=j\omega l, y=j\omega c \Rightarrow v = v(0)e^{\pm j\omega\sqrt{lc}x}$$

For a sine wave we have: $v = v(0)e^{j\omega(t\pm\sqrt{lc}x)}$ $v = \frac{1}{\sqrt{lc}}$


Wave traveling with velocity v in positive or negative direction along the line

Characteristic impedance: $Z_c = \sqrt{\frac{l}{c}} = Z_0$ Typical value 50Ω
(Real in lossless case) (20...300 Ω)

Also note that $c = \frac{1}{vZ_0}$

Modeling transmission lines

 Interpretation of signal transfer, an example:




Two waves:

$$v_{1,2} = v_+ + v_-$$

Open end: $i_2 = i_{2+} + i_{2-} = 0$

$$v_2 = -i_2 Z_0 = i_{2+} Z_0 = v_{2+}$$

Source end: $v_2 / i_2 = Z_0$

 

Modeling transmission lines

Interpretation for a lossy line with simple series resistance:

$$z=j\omega l+r, y=j\omega c \Rightarrow v = v(0)e^{\pm\sqrt{(j\omega l+r)j\omega c}x}$$

For small r we have:

$$\sqrt{j\omega c(j\omega l+r)} \approx \sqrt{-\omega^2 lc} \left(1 - j \frac{r}{2\omega l}\right) = j\omega\sqrt{lc} - \frac{r}{2Z_0}$$

Wave attenuated along line

$$v = v(0)e^{-j\omega\sqrt{lc}x} e^{-\frac{r}{2Z_0}x}$$

Characteristic impedance complex


$$Z_c = \sqrt{\frac{j\omega l+r}{j\omega c}}$$

Modeling transmission lines

Skin effect loss

Higher frequencies - skineffekt
Fields penetrate metal to skin-depth δ
Resistance per unit length, r:

$$r = r_s \sqrt{\omega}$$

 

Including current phase and low frequency resistance:

$$r = r_{DC} + r_s(1+j)\sqrt{\omega}$$


Frequency dependence gives rise to signal distortion

Modeling transmission lines

Dielectric loss

Higher frequencies – dielectric loss
Loss due to molecular movements
(Relaxation loss)
 
$$\epsilon = \sum_i \frac{a_i}{1 + j\omega\tau_i}$$



Dielectric constant, ϵ , may be complex

Frequency dependence gives rise to signal distortion

Most relevant in circuit boards at >10GHz

Modeling transmission lines


Converting to time domain

$$H = e^{-\sqrt{(j\omega+r)}j\omega c x} \quad \begin{array}{l} \text{Voltage transfer function} \\ \text{Complex and frequency dependent } r \text{ and } c \text{ (through } \epsilon) \end{array}$$

$$g = \frac{1}{2}(1 + \text{erf}(a_1(t - t_1))) \quad (\text{Step response in time domain})$$

$$v(t) = \text{ifft}(HG) \quad (\text{Step in time domain})$$

Step response

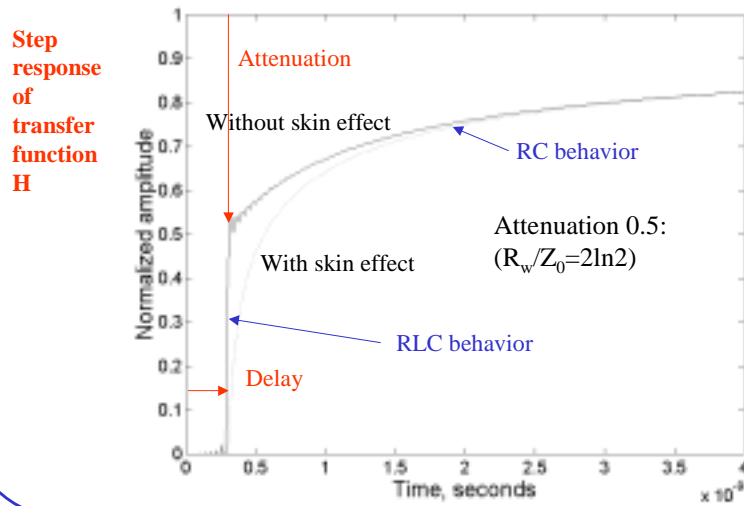

Christer Svensson, VLSI Design 2002

15

Step response

Large attenuation ($R_w/Z_0 \gg 2\ln 2$):

We have a pure RC behaviour
We have very small skin effect

Low attenuation, $R_w/Z_0 \ll 2\ln 2$:


We have an RLC behavior (still with loss)
Skin effect dominates resistance

(Note that transfer between RC and RLC resp. DC resistance and skin effect resistance happens to occur at the same point)

Christer Svensson, VLSI Design 2002

16

Step response of wire with driver

 

(Solve circuit equations with two waves)

$$v_{out} = \frac{2H}{1 + H^2 + \frac{Z_0}{Z_c}(1 - H^2)} v_{step}$$

For $Z_c = Z_0$:

$$v_{out} = 2H v_{step}$$

Step response same as for H

Step response of wire with driver


Pure RC case (very large loss)

$$H = e^{-\sqrt{j\omega r}x} \quad Z_c = \sqrt{\frac{r}{j\omega c}}$$


Step response must
be calculated from
full expression

$$v_{out} = \frac{2Hv_{step}}{1 + H^2 + \frac{Z_0}{Z_c}(1 - H^2)} \approx \frac{2Hv_{step}}{1 + H^2} \approx \frac{v_{step}}{1 + \frac{j\omega R_w C_w}{2}}$$

Good approximation:
(lumped model)

 

Step response of wire with driver

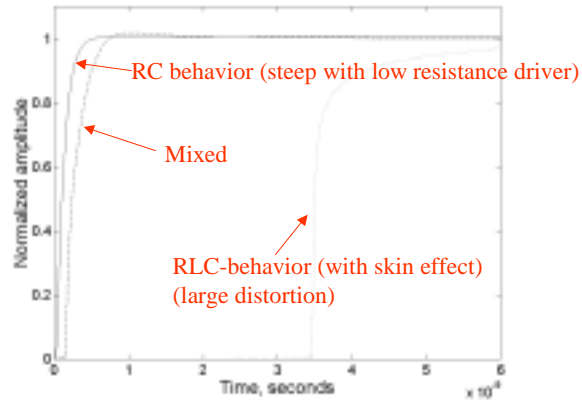

Christer Svensson, VLSI Design 2002

19

Wire performance

Delay or latency, LC-wire

Delay mainly through velocity, $t_d = vL$, L =wire length

$$v = \frac{1}{\sqrt{lc}} = \frac{c_0}{\sqrt{\epsilon_r}}$$

c_0 velocity of light in vacuum, ϵ_r dielectric constant (square of refractive index)
Note, no higher velocity is possible.

Only difference to optics is the value of refractive index (about 1.9 resp. 1.5)


Christer Svensson, VLSI Design 2002

20

Wire performance

Delay or latency, RC-wire

 RC-wire: Delay mainly through RC charging time, for 50% of final value:




If we assume that a practical wire has a fixed aspect ratio (w/t), we have:


$$t_d = a_{RC} \frac{L^2}{A} \quad \text{A is wire cross section}$$

Wire performance

Delay or latency, RC-wire with driver


 


 For long wires, delay may be reduced by repeaters:



Wire performance

Capacity or maximum data rate

  

Eye opening = $2S(T)-1$, $S(t)$ step response, T symbol time
 We need a minimum opening for safe data detection, say 64%
 For long wires we may afford a simple equalizer, allowing 0%

Wire performance

Capacity or maximum data rate

RC-wire: Step response: $S(T) = 1 - e^{-\frac{2T}{R_w C_w}}$

Eye opening of 64% yields $S(T)=0.82$ or $T=0.85R_w C_w$

Max data rate $B = \frac{1}{T} = b_{RC} \frac{A}{L^2}$

RLC-wire: Step response (skin effect): $S(T) = 1 - \operatorname{erf}\left(\frac{\sqrt{\rho\mu_0 L}}{2Z_0 w \sqrt{T}}\right)$

Max data rate, $B = b_{RLC} \frac{A}{L^2}$

Wire performance

Capacity or maximum data rate


$$B = b \frac{A}{L^2}$$

RC-model (eye opening 64%)	$b_{RC} = 5.3 \cdot 10^{17}$ b/s
RC-model (eye opening 0%)	$b_{RC0} = 1.3 \cdot 10^{18}$ b/s ($= 1/a_{RC}$)
RLC model (eye opening 0%)	$b_{RLC0} = 4.3 \cdot 10^{17}$ b/s

For a bus: $A = \Sigma A$


Assumptions: $Z_0 = 50\Omega$, Copper, Silicon dioxide

Estimated data rates

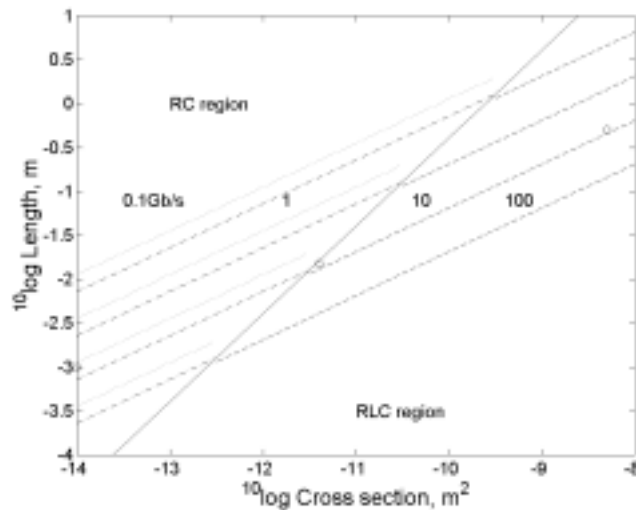

Wire performance

Crosstalk

 


$$\text{Peak crosstalk} \approx \frac{\pi}{4} \frac{C_m}{C_{grd} + C_m}$$

Realistic wires (aspect ratio 3) need $w_{m-m} \sim 1.5w_m$ to limit crosstalk to 20%

(J. A. Davis and J. D. Meindl, IEEE Trans. Electronic Devices, vol. 47, p. 2078, 2000)

Wire performance

Power consumption

 

Inverter with output resistance Z_0

Random data

$T_D = L/v$


Data rate: $f = 1/T$

Current consumption:	$\bar{I} = \frac{1}{4} f C V_0$	For $2T_D < T$
	$\bar{I} = \frac{V_0}{8Z_0}$	For $2T_D > T$

Power Consumption:	$P_{wire} = \bar{I} V_0$	V_0 is supply
	$P_{wire} = \bar{I} V_{dd}$	Separate supply

Wire performance

Power optimum voltage swing

 

Using reduced swing to save power needs an amplifier for restoring swing to V_{dd}

$$P = P_{wire} + P_{ampl}$$

The total power shows a minimum for a particular swing, V_{opt}


Wire performance

Power optimum voltage swing (Example)

Process: (Inverters as amplifiers)
 $V_{dd}=1.3V$, $V_T=0.3V$, $G_{max}=5$

General:
 $C_L=10fF$, $C_w=1pF$, $f_c=1GHz$,
 $\alpha=0.05$ and 0.25

α =activity (f/f_c)

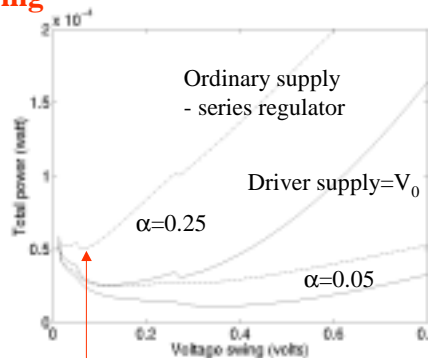

Optimum swing ~ 60 mV @ $\alpha=0.25$; power saving 8x (Using ordinary supply); two stage amplifier

Wires in real systems

We will examine three cases and draw some practical conclusions from these

Wires on circuit boards

Global wires on chip

Local wires on chip

Wires in real systems

Wire on circuit board:

Far into RLC region: $A=5 \cdot 10^{-9} \text{ m}^2$, $L=0.5\text{m}$ $B=10\text{Gb/s}$
Delay=3.3ns (velocity of light in polymer)


Upper level chip wire:

At borderline: $A=4 \cdot 10^{-12} \text{ m}^2$, $L=1.5\text{cm}$ $B=20\text{Gb/s}$
Delay \approx 100ps (RLC-model)

Lower level chip wire

Far into RC region: $A=10^{-14} \text{ m}^2$, $L=1\text{mm}$, $B=5\text{Gb/s}$
Delay=80ps


Wires in real systems

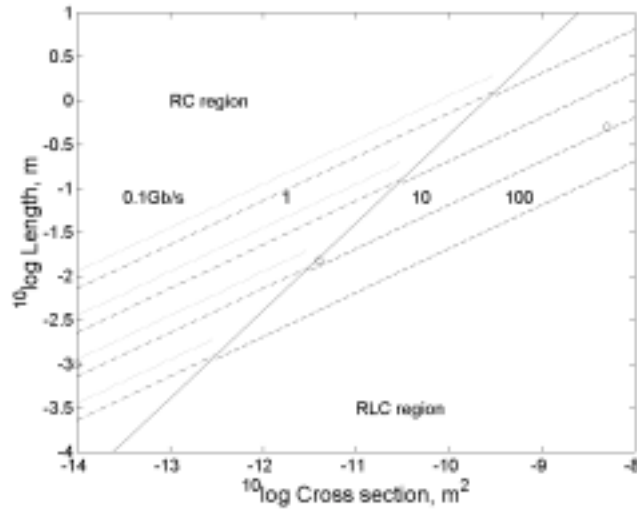

Christer Svensson, VLSI Design 2002

33

Wires in real systems

 

Christer Svensson, VLSI Design 2002

34

Chip I/O capacity


Typical board wire: $0.25\text{mm} \times 20\mu\text{m} = 5 \cdot 10^{-9}\text{m}^2$
10Gb/s 0.5m, more than a full board!

Chip edge capacity: Bus effective cross section: $2\text{cm} \times 20\mu\text{m} / 2.5$
(assuming chip edge 2cm and wire to wire distance $1.5 \times$ (wire width)
length 10cm
gives bus capacity $B = 6.8\text{Tb/s}$
Can be implemented with 340 wires at 20Gb/s each.
Pitch $58\mu\text{m}$, quite possible
Total chip I/O: 27.2Tb/s (using 4 edges)

Christer Svensson, VLSI Design 2002

35

Optical example

 

Example from literature: 4Tb/s for 4cm^2 area
Total power 4W (my optimistic view)
(Electrical case estimated optimal power 0.1W at 120mV swing)
(Kibar, VanBlerkom, Fan, Esener, J Lightwave Techn., vol. 17, p. 546, 1999)

Christer Svensson, VLSI Design 2002

36

On-chip global

Keeping full light velocity needs $R_w < Z_0 2 \ln 2$
For 2cm chip, max length (Manhattan) 4cm
Then we need $A = 10^{-11} \text{m}^2$
Not unrealistic; example $3.2 \times 3.2 \mu\text{m}^2$
(Microprocessor of today, $2.2 \mu\text{m}$ thick outer metal)
 $B = 8 \text{Gb/s}$

Bus capacity across chip: $A = 2 \text{cm} \times 3 \mu\text{m} / 2.5$ $L = 2 \text{cm}$
 $B = 77 \text{Tb/s}$ (compare external edge: 6.8Tb/s)
(2700 wires of $3 \mu\text{m}$ at 28Gb/s ; total power 2.7W
@ 90mV swing)

On-chip local

Future processes, feature size $f = 0.1 - 0.035 \mu\text{m}$
wire cross section $\sim 3f^2$, for $0.1 \mu\text{m}$: $3 \cdot 10^{-14} \text{m}^2$
 10Gb/s up to 1.25mm length
 1mm wire will have a delay of 26ps (26% of 10GHz clock cycle)

We may use **10GHz clock frequency** in fully synchronous block
of diameter 1mm . Such a block can contain **250,000 gates**.
(Compare to Sylvester and Keutzer 50-100 kgates)

Note that diameter scales as f^2 ; number of gates as f^2
so 250 kgates is kept until $0.035 \mu\text{m}$ (or further) at 10GHz .

Clock distribution

For clock distribution the only critical issue is to **distribute a constant frequency** with equal delay to each target

Using a balanced H-tree allows equal delay
H-tree over $2 \times 2 \text{cm}^2$ chip, longest path $< 2 \text{cm}$

$A = 10^{-11} \text{ m}^2$ (as above), $L = 2 \text{cm}$, total delay $\sim 130 \text{ps}$

$A = 10^{-11} \text{ m}^2$, $L = 2 \text{cm}$: 50% attenuation at **22GHz** ($T = 45 \text{ps}$)

Conclusions

Electrical interconnects are still very effective

We may have a total I/O capacity of 25Tb/s.
(Optical can not compete at short distances (on board))

An upper metal may carry 70Tb/s across chip, with a delay corresponding to light velocity

Full synchronism can be used at 10GHz clock in blocks containing $> 200 \text{k}$ gates (diameter 1mm in $0.1 \mu\text{m}$ process)

On-chip global clock distribution up to 20GHz possible

References

- W. J. Dally and J. W. Poulton, Digital Systems Engineering, Cambridge university press, 1998.
- C. Svensson, Electrical Interconnects Revitalized, manuscript (see www.ek.isy.liu.se/~christer/InterconnectManuscript.pdf)
- D. Sylvester and K Keutzer, Getting to the Bottom of Deep Submicron, Proc. Of Int. Conf. on Computer Aided Design, 1998
- D. A. B. Miller and H. M. Özatkas, Limit to the Bit-Rate Capacity of Electrical Interconnects from Aspect Ratio of System Architecture, J. Parallell. Distrib. Comput., vol 41, p. 52, 1997.
- C. Svensson, Optimum Voltage Swing on On-Chip and Off-Chip Interconnects, IEEE Journal of Solid-State Circuits , Vol: 36, p. 1108 –1112, 2001.
- C. Svensson and G. Dermer, Time Domain Modeling of Lossy Interconnects, IEEE Transactions on Advanced Packaging, Vol. 24, p 19, 2001.