

## 5. BASIC CIRCUIT ELEMENTS

5.1 a

5.2 a) According to Theorem 5.1 we have

A system that initially is at rest and contains no stored energy is passive if the energy,  $w(t)$ , which is supplied to the system, is always non-negative. That is, for all ports we have

$$w(t) = \sum_{\text{all ports}} Re \int_{-\infty}^t i^*(\tau)v(\tau)d\tau \geq 0 \quad \forall t \quad (5.1)$$

and for a resistor we have  $v(t) = R i(t)$ . We get

$$w(t) = Re \int_{-\infty}^t i^*(\tau)Ri(\tau)d\tau = Re \int_{-\infty}^t R i^*(\tau)i(\tau)d\tau \geq 0$$

for all  $t$  and om  $R > 0$ . Hence, a passive element.b) We have for an inductor  $v(t) = L \frac{d}{dt}i(t)$  which yields  $w(t) = Re \int_{-\infty}^t i^*(\tau)L \frac{d}{dt}i(\tau)d\tau = \frac{L}{2}i^2(t) \geq 0$  if  $L \geq 0$ . The stored reactive energy in an inductor depends only on the current at time  $t$ .Inductors (including time varying) are lossless since the stored reactive energy from a current that flows under a finite time period, i.e.,  $i(\infty) = 0$ , is

$$w(t) = Re \int_{-\infty}^{\infty} i^*(\tau)L \frac{d}{dt}i(\tau)d\tau = \lim_{t \rightarrow \infty} \frac{L}{2}i^2(t) = 0.$$

c) For a capacitor we have  $i(t) = C \frac{d}{dt}v(t)$  and  $w(t) = Re \int_{-\infty}^t v^* \tau C \frac{d}{dt}v \tau dt = \frac{C}{2}v^2(t) \geq 0$  if  $C \geq 0$ .

Capacitors are also lossless.

d) active according to b)

e) active according to c)

f) a negative resistor can according to a) generate energy, i.e., it is active.

5.3 a) For a two-port with a series impedance we have  $V_1 = Z I_1 + V_2$  and  $I_1 = -I_2$  and  $V_1 = V_2 + Z(-I_2)$ 

$$I_1 = 0 + 1(-I_2) \quad \text{which can be written:} \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \mathbf{K}_{series} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

b) For a two-port consisting of a shunt impedance we have  $V_1 = V_2$  and  $V_1 = Z(I_1 + I_2)$  and  $I_1 = V_1/Z - I_2$ 

$$= V_2/Z + 1(-I_2) \quad \text{and we get the } \mathbf{K} \text{ matrix, } \mathbf{K}_{shunt} = \begin{bmatrix} 1 & 0 \\ 1/Z & 1 \end{bmatrix}$$

$$5.4 \quad \mathbf{K}_{KCVS} = \begin{bmatrix} 1 & 0 \\ A & 0 \end{bmatrix}, \mathbf{K}_{KCCS} = \begin{bmatrix} 0 & 1 \\ 0 & g \end{bmatrix}, \mathbf{K}_{KCVS} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}, \mathbf{K}_{KCCS} = \begin{bmatrix} 0 & 0 \\ 0 & 1/g \end{bmatrix}$$

$$5.5 \quad \mathbf{K}^{-1} = \frac{1}{AD - BC} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix}$$

5.6 For a two-port we have according to its definition of the  $\mathbf{K}$  matrix

$$V_1 = AV_2 + B(-I_2)$$

$$I_1 = CV_2 + D(-I_2)$$

and  $V_{in} = R I_1 + V_1$  and  $V_2 = -R_2 I_2$  where the currents are defined into the two-port. Eliminationyields  $I_2 = -V_2/R_2$  and using the equations above yields  $V_1 = AV_2 + BV_2/R_2 = (A + BR_2)V_2$  and  $I_1 = CV_2 + DV_2/R_2 = (C + D/R_2)V_2$  and we get  $V_{in} = R I_1 + V_1 = R_1(C + D/R_2)V_2 + (A + BR_2)V_2$  and

$$\text{finally we get } H(s) = \frac{V_2}{V_{in}} = \frac{1}{\frac{R_1}{V_{in}} + \frac{B}{A + CR_1 + D \frac{R_1}{R_2}}}$$

5.6 The  $\mathbf{K}$  matrix for the LC ladder is

$$\mathbf{K}_{LC} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & Z_2 \end{bmatrix} = \begin{bmatrix} Z_1 + 1 & Z_1 \\ Z_2 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_3 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} Z_1 + 1 & ((Z_1 + 1)Z_3 + Z_1) \\ 1 & Z_3 + 1 \end{bmatrix} = \begin{bmatrix} C_2 L_1 s^2 + 1 & (C_2 L_3 L_1 s^3 + (L_1 + L_3)s) \\ C_2 s & C_2 L_3 s^2 + 1 \end{bmatrix}$$

Insertion into the expressions derived in Problem 5.6 yields the transfer function.

$$H(s) = \frac{R_L}{C_2 L_3 L_1 s^3 + (L_1 R_L + L_3 R_3) C_2 s^2 + (L_1 + L_3 + C_2 R_L R_3)s + R_L} \quad \text{and}$$

$$H(s) = \frac{5.0505010^8}{s^3 + 2000s^2 + 2010101s + 1.01010110^9} = \frac{5.0505010^8}{(s + 1000)(s + 500 - j871.83)(s + 500 + j871.83)} = \frac{5.0505010^8}{(s + 1000)(s^2 + 1000s + 1010101)}$$

The DC gain for the filter is  $H(0) = \frac{R_L}{R_s + R_L}$ . Note that here the transfer function is different from the normal transfer function, i.e., the ratio of the output and input voltage is maximally  $R_L/(R_s + R_L)$ . The normal transfer function is normalized to be maximally equal to unity.

$$5.7 \quad \mathbf{K} = \begin{bmatrix} 1 & sL_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ sC_2 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & sL_3 \\ sC_4 & 1 \end{bmatrix} \begin{bmatrix} 1 + s^2 L_1 C_2 s L_1 & 1 + s^2 L_3 C_4 s L_3 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} 1 + s^2 L_1 C_2 s L_1 & 1 + s^2 L_3 C_4 s L_3 \\ sC_2 & 1 \end{bmatrix} \begin{bmatrix} C_4 L_3 s^2 + 1 & C_4 L_5 L_1 s^3 + (L_3 + L_5)s \\ C_4 s & C_4 L_5 s^2 + 1 \end{bmatrix} = \begin{bmatrix} (C_4 L_3 s^2 + 1)(1 + s^2 L_1 C_2) + C_4 L_1 s^2 s L_1 (C_4 L_5 L_1 s^3 + (L_3 + L_5)s) & (1 + s^2 L_1 C_2) \\ sC_2 (C_4 L_5 s^2 + 1) + C_4 s & sC_2 (C_4 L_5 L_1 s^3 + (L_3 + L_5)s + C_4 L_5 s^2 + 1) \end{bmatrix}$$

$$= \begin{bmatrix} 3.2358s^4 + 5.2358s^2 + 1 & 1.9997s^5 + 5.2356s^3 + 3.236s \\ 5.2358s^3 + 3.236s & 3.2358s^4 + 5.2358s^2 + 1 \end{bmatrix}. \text{ Hence, we get}$$

$$H(s) = \frac{1}{\frac{R_s}{A + CR_1 + DR_2}} = \frac{1}{1.9997s^5 + 6.4715s^4 + 10.471s^3 + 10.472s^2 + 6.472s + 2}$$

$$= \frac{1}{1.9997(s^2 + 0.61807s + 1)(s^2 + 1.6181s + 1)(s + 1)}$$

Note that the pole radius is equal for all the poles in a Butterworth filter:

5.8 a We have for an ideal operational amplifier

$$\begin{aligned} V_1 &= V_2 \\ R_1 I_1 &= R_3 I_2 \\ V_2 &= -R_2 I_2 \end{aligned}$$

where  $I_1$  and  $I_2$  are the currents are into the two-port.

We get the chain matrix  $\begin{bmatrix} V_1 & I_1 \\ 0 & -R_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & -R_1 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$  which do not correspond to a reciprocal two-port since

$AD - BC \neq 1$ . Furthermore it is active since  $A \neq 1/D$ .

The two-port is a NIC (Negative Impedance Converter) with  $n_1 = 1$  and  $n_2 = R_3/R_1$ . The particular circuit is denoted INIC where  $I$  refer to current since port voltages are equal and  $I_1 = (R_3/R_1)I_2$ . Also VNIC circuits exist where the input currents are equal and the port voltages are  $V_1 = kV_2$ .

b) We get from the equations above:  $Z_{in} = -(R_1/R_3)R_2$

The input impedance to a NIC is  $Z_{in} = -(R_1/R_3)Z_2$  where  $Z_2$  is the load impedance. The right port is open-circuit-stable and the left port is short-circuit-stable, i.e., the two NICs stable if they have a high or low load impedances, respectively.

5.9 a In the same ways as in Problem 5.9 a we get the  $\mathbb{K}$  matrices for the two NICs

$$\begin{bmatrix} 1 & 0 \\ 0 & -Z_2 \\ 0 & -Z_1 \end{bmatrix} \text{ and } \begin{bmatrix} 1 & 0 \\ Z_4 & 0 \\ 0 & -Z_3 \end{bmatrix}$$

and  $\mathbb{K}$  matrices for the two cascade connected NICs yields

$$\begin{bmatrix} V_1 & I_1 \\ 0 & -Z_2 \\ 0 & -Z_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Z_4 & 0 \\ 0 & -Z_3 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$$

Furthermore, we have  $V_2 = -Z_5 I_2$ , which with the

$$\mathbb{K} \text{ matrix yields } Z_{in} = \frac{V_1}{I_1} = \frac{V_2}{\frac{Z_1 Z_3}{Z_2 Z_4} I_2} = \frac{Z_1 Z_3}{Z_2 Z_4} Z_5$$

For the  $\mathbb{K}$  matrix we have  $A = 1, B = C = 0$  and  $D = \frac{Z_1 Z_3}{Z_2 Z_4}$

$= (Z_2 Z_4)/(Z_1 Z_3)$ . Hence, the circuit is a positive impedance converter (PIC). It is nonreciprocal since  $AD - BC \neq 1$  if  $D \neq 1$  and active if  $A \neq 1/D$ .

b) The  $\mathbb{K}$  matrix is  $\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$ , i.e.,  $V_1 = V_2$  and  $I_1 = -I_2$  which represent a direct connection of the two ports.


5.10 Consider the circuit that consist of three cascaded two-ports. Using the notation according to

the figure we get the chain matrix,  $\mathbb{K}_1$  for series resistor  $R_1$ :  $V_1 = R_1 I_1 + V_2$  and  $I_1 = -I_2$  which gives

$$\begin{bmatrix} V_1 & I_1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$$

In Problem 5.8 a we derived the chain matrix for the inner two-port  $\mathbb{K}_2$  and with

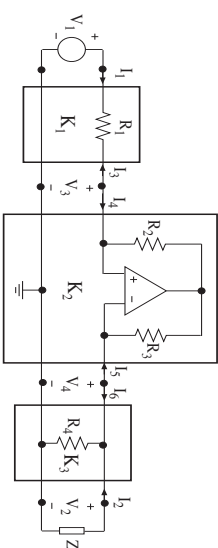the new notation we get  $\begin{bmatrix} V_3 & I_3 \\ 0 & R_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & -R_2 \end{bmatrix} \begin{bmatrix} V_4 & I_4 \\ -I_4 & -I_4 \end{bmatrix}$



For the last two-port we have  $V_2 = R_4(I_6 + I_2)$  and  $V_4 = V_2$ . The chain matrix,  $\mathbb{K}_3$  for the parallel

$$\text{resistor } R_4 \text{ is } \begin{bmatrix} V_4 & I_4 \\ 0 & -R_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & -R_4 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$$

The resulting chain matrix is obtained by successively multiply the three  $\mathbb{K}$  matrices, i.e.,

$$\begin{bmatrix} V_1 & I_1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_3 & I_3 \\ -I_3 & -I_3 \end{bmatrix} = \begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ R_3 & -I_5 \end{bmatrix} \begin{bmatrix} V_4 & I_4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & -R_2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & -R_4 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$$


where  $I_3 = -I_4$  and  $I_5 = -I_6$ . We get

$$\begin{bmatrix} V_1 & I_1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & R_1 \\ 0 & -R_3 \\ 0 & -R_2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} R_3 R_1 & R_3 R_1 \\ R_2 R_4 & R_2 \\ -R_2 & -R_2 \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}$$

and if  $R_1 = R_2 = R_3 = R_4 = R$  we get

$$\begin{bmatrix} V_1 & I_1 \\ 0 & -R \\ -R & -R \end{bmatrix} \begin{bmatrix} V_2 & I_2 \\ -I_2 & -I_2 \end{bmatrix}, \text{ i.e., } V_1 = R I_2 \Rightarrow I_2 = V_1/R \text{ and } I_1 = -V_2/R + I_2 \Rightarrow V_1 = R I_1 + V_2$$

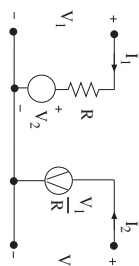The circuit is a voltage controlled ( $V_1$ ) current source ( $I_2$ ) where the current is independent of the impedance  $Z$ . The circuit can therefore be used as a voltage to current converter.



5.11 For the inverting amplifier we get  $Z_1^{-1}(V_1 - V_2) + Z_2^{-1}(V_2 - V_2) = 0$

$$A(V_+ - V_-) = V_2 \text{ and } V_1 = -\frac{Z_2}{Z_1 + Z_2} V_+$$


$$\text{and } H(s) = -\frac{R_2}{R_1 + R_2} = -\frac{10^4}{210^4} = -\frac{10^7}{s + 1.00001 \cdot 10^7}$$

where

$$A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}} = \frac{2 \cdot 10^7}{s + 10^7}$$

We get a real pole at  $s_p = -10.0001$  Mrad/s. The bandwidth (3 dB) = 10.0001 Mrad/s. Note it is not always that we define the band edge at the 3-dB edge.

We get for the non-inverting amplifier

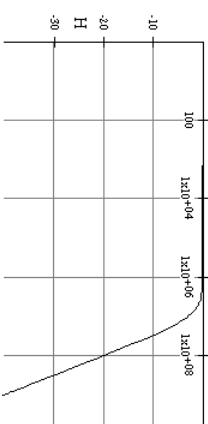

$$\begin{cases} V_- = \frac{Z_1}{Z_1 + Z_2} V_2 \\ V_+ = V_1 \\ A(V_+ - V_-) = V_2 \end{cases} \text{ which yields } H(s) = \frac{Z_1 + Z_2}{Z_1 + \frac{Z_2}{A}} = \frac{2 \cdot 10^7}{s + 1.00001 \cdot 10^7}. \text{ Hence, the same}$$

frequency response as for the inverting amplifier but with the DC gain,  $H(0) = +2$ . Also in this case, we get a real pole at  $s_p = -10.0001$  Mrad/s. The bandwidth (3-dB) = 10.0001 Mrad/s is in this case the same for the inverting and non-inverting amplifier.

- b) For the inverting amplifier we have  $H(s) = -\frac{10^5}{10^4 + 11 \cdot 10^4 s} = -\frac{1.8182 \cdot 10^7}{s + 1.81828 \cdot 10^6}$ . We get a real pole at  $s_p = -1.81828$  Mrad/s and bandwidth (3 dB) = 1.81828 Mrad/s. The DC-gain is  $H(0) = -9.99945$

For the non-inverting amplifier we get  $H(s) = \frac{2 \cdot 10^7}{s + 1.81828 \cdot 10^6}$ . We get the same frequency response as for the inverting amplifier but with the DC-gain,  $H(0) = +10.9994$ .

- c) For the inverting amplifier is the case with  $R_1 = \infty$  not relevant since it leads to a non-working amplifier. For the non-inverting amplifier we get  $H(s) = \frac{A}{A + 1} = \frac{2 \cdot 10^7}{s + 2.00001 \cdot 10^7}$ . The DC gain becomes,  $H(0) = +0.999995$  and bandwidth 20.0001 Mrad/s. A comparison yields

Inverting amplifier (H(0))	Bandwidth, Mrad/s
-1	10.0001
-10	1.81828
Non-inverting amplifier (H(0))	Bandwidth, Mrad/s
1	20.0001
2	10.0001
11	1.81828


Hence, the bandwidth reduces rapidly with increasing gain and the non-inverting amplifier have a slightly larger bandwidth at the same gain compared to the inverting amplifier.

5.12 The resistor  $r$  is used to compensate for the offset-error that occur at the input of the amplifier due to the bias currents goes through different DC-impedances. Note that there are several cause for the off-set voltage. If both inputs has the same bias-currents and sees the same DC-impedance, then the voltage at the amplifiers input will be zero. Typically, the resulting offset-error will in practice be reduced with a factor of 4 if the DC impedance are the same. For both the inverting amplifier and for the non-inverting amplifier we shall select  $r = R_1/R_2$ . If  $Z_2$  is a capacitance we select  $r = R_1$ .

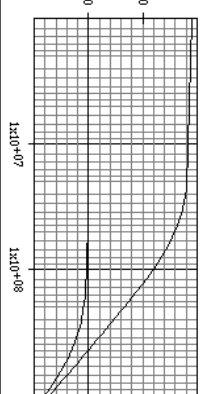5.13 The operational amplifier is used in the circuit for the non-inverting amplifier. We have


$$H(s) = \frac{Z_1 + Z_2}{Z_1 + \frac{Z_2}{A}} = \begin{cases} \frac{1}{A} + 1 & \text{for Gain} = 1 \\ 10 \frac{A}{A + 10} & \text{for Gain} = 10 \text{ med } Z_2 = 9Z_1 \end{cases} \text{ and for operational amplifier}$$

We get  $A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}}$ . Let  $A(s)$  in  $H(s)$  and equate the numerators real and imaginary parts, which yields the amplifiers 3-dB-band edge. We get  $A_0 = 80$  and  $\omega_{3dB} = 5.5555$  Mrad/s, i.e.,  $f_{3dB} = 884.2$  KHz.



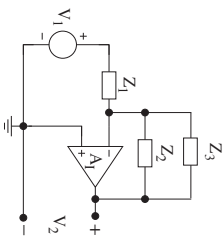- 5.14 According to Problem 5.11 we have  $V_2 = -\frac{R_2}{R_1 + R_2} \frac{V_1}{A}$ . For high frequencies, i.e.,  $\omega \gg \omega_{3dB}$ . We have  $A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}} \approx \frac{A_0 \omega_{3dB}}{s}$ . Inserting  $A(s)$  into the

above gives  $H(s) = -\frac{R_2}{(R_1 + R_2)s} \frac{1}{\omega_1}$ . We replace the original resistor  $R_2$  with an impedance  $Z_3$  so that  $H(s) = -\frac{R_2}{(R_1 + R_2)s} = -\frac{Z_3}{R_1 + \frac{R_2}{\omega_1}}$ . This correspond to an inverting amplifier with an ideal operational amplifier with gain  $A_1 = \infty$ . A resistor  $R_2$  parallel with a capacitor  $C_3$  has the impedance  $\frac{R_2}{\omega_1 R_2 C_3 + 1}$ . We get  $Z_3 = \frac{\omega_1 R_2 R_1}{\omega_1 R_1 + (R_1 + R_2)s} = \frac{R_2}{C_3 R_2 s + 1}$  and  $C_3 = \frac{(R_1 + R_2)}{\omega_1 R_2 R_1}$ . For example,  $Z_1 = R_1 = 10$  k $\Omega$  and  $Z_2 = R_2 = 100$  k $\Omega$  and operational amplifier with  $A_0 = 2 \cdot 10^5$ ,  $\omega_{3dB} = 200$  rad/s,  $\omega_1 = 40$  Mrad/s yields  $C_3 = \frac{10 + 100}{4 \cdot 10^7 \cdot 10 \cdot 100} = 2.75 \cdot 10^{-12}$ . The parallel capacitor shall have the capacitance 2.75 pF.



Note that the correction admittance should be equal to the sum of all admittances that are connected to the (-)input divided by  $\omega_1/s$ .

- 5.15 According to the example above, the correction admittance  $Y_3$  equals the sum of all admittances connected to the (-)input divided by  $GB/s$ . In this case,

$$Y_3 = \frac{(Y_1 + Y_2)}{GB} = \frac{(1/R + sC)}{GB} = \frac{s}{RGB} + \frac{s^2 C}{RKB + GB}$$

Identification yields  $C_1 = \frac{1}{RKB}$  and  $D = \frac{C}{GB}$ .

In order to correct for the finite  $GB$ , an extra correction capacitor and an supercapacitor is required. For example,  $R = 10$  k $\Omega$  and  $C = 100$  nF and operational amplifier have  $A_0 = 2 \cdot 10^5$ ,  $\omega_{3dB} = 200$  rad/s,  $GB = 40$  Mrad/s we get  $C_1 = 2.5 \cdot 10^{-15} = 2.5$  fF (this is a very low value) and  $D = 100$  nFs. Of course, this solution is not efficient in practice.

- 5.15 For the circuit we have

$$\begin{cases} (V_1 - V_2) + sC(V_2 - V_2) = 0 \\ \frac{R}{A(V_+ - V_-)} = V_2 \\ V_+ = 0 \end{cases} \quad \text{Elimination gives } H(s) = -\frac{\frac{1}{sC}}{R + \frac{1}{sC}} = -\frac{1}{sRC + \frac{1+sRC}{A}}. \text{ With}$$

$$A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}} \approx \frac{GB}{s} \text{ we get } H(s) = -\frac{GB}{\left(s + GB + \frac{1}{RC}\right) sRC}$$

We get, if the operational amplifier gain is large,  $H(s) = -\frac{1}{sRC}$ .

We get, with the values above,  $H(s) = -\frac{10^{14}}{(s + 20 \cdot 10^6)s}$ . The pole  $s_p = -20 \text{ Mrad/s}$  is far from the

$j\omega$ -axis and do not effect integrator significantly. With  $A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}}$  without any approximation

we get  $H(s) = -\frac{10^{14}}{(s + 20 \cdot 10^6)(s + 50)}$ , i.e., the pole at  $s = 0$  have moved into the LHP. A resistor,  $r$

$= R$ , should be used between ground and (+)-input in order to minimize the effect of the bias currents.

5.16 We get for the node currents

$$\begin{cases} \frac{R_1}{(V_1 - V_+)} - sC V_+ + \frac{(V_2 - V_+)}{R_2} = 0 \\ \frac{(V_2 - V_-)}{R_3} - \frac{V_-}{R_4} = 0 \end{cases} \quad \text{and}$$

$$\frac{V_2}{V_1} = \frac{(R_3 + R_4)R_2}{sCR_1R_2R_4 - R_1R_3 + R_2R_4 + \frac{(R_3 + R_4)(sCR_1 + 1)R_2 + R_1}{A}} \quad \text{and with } R_1 = R_2 = R_3 = R_4 = R$$

we get  $H(s) = \frac{2}{sRC + 2(sRC + 2)\frac{1}{A}}$  and with an ideal operational amplifier we get  $H(s) = \frac{2}{sRC}$ . The

circuit is called **Deboo's integrator**. With the element values used above we get

$H(s) = \frac{10^{14}}{(s + 80)(s + 2.5 \cdot 10^7)}$ . The pole  $s_p = -25 \text{ Mrad/s}$  is far from the  $j\omega$ -axis and do not effect

integrator significantly while the pole  $s_p = -80 \text{ rad/s}$  is more important and it lies further away compared to the real pole in the Miller-integrator in Problem 5.15. The most important difference is that Deboo's integrator is positive.

With an ideal operational amplifier we get  $H(s) = \frac{(R_3 + R_4)R_2}{sCR_1R_2R_4 - R_1R_3 + R_2R_4}$  which can be written

$$H(s) = \frac{(R_3 + R_4)R_2}{CR_1R_2R_4} \frac{1}{s + \frac{1}{CR_1R_2R_4} \left( \frac{R_1}{R_2} - \frac{R_4}{R_3} \right)}. \text{ The pole is } s_p = \frac{1}{CR_1} \left( \frac{R_3}{R_2} - \frac{R_4}{R_3} \right).$$

We must therefore select  $\frac{R_4}{R_3} \gg \frac{R_1}{R_2}$  (pole in the LHP). Unfortunately we get a large deviation in the phase response. The

input impedance is frequency independent. The circuit is a NIC that is connected to the  $R_1C$  section, compared with Problem 5.8 a, and realize a en negative resistor  $R_0$  in parallel with  $C$  where  $R_0 = -$

$$R_2R_4R_3 = -R. \text{ The voltage over the capacitor is } V_C = \frac{R_1V_1}{R_1 + Z} \text{ where } Z = 1/sC // (-R_0) \Rightarrow$$

$Z = \frac{-R_0}{1 - sCR_0}$  which yields  $H_C = \frac{1}{sCR}$  and the operational amplifier gives a gain with a factor 2.

5.17 a)  $H(s) = \frac{-1}{sRC}$  The integrator is less sensitive for the operational amplifiers finite  $GB$ .

b)  $H(s) = \frac{+1}{sRC} \frac{R_2}{R_1}$ , Positive integrator.

c)  $H(s) = \left( \frac{1 + R_1C_1}{1 + R_2C_2} \right) \frac{+1}{sRC} = \frac{+1}{sRC}$  if  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$ . The input impedance to the integrator is  $Z_{in} = R + 1/sC$  and the circuit must have a low impedance signal source.

d)  $H(s) = \frac{+2}{sRC}$  The integrator is less sensitive for the operational amplifiers finite  $GB$ .

5.18

5.19

5.20 For a transistor we have:  $I = g_m(V_+ - V_-)$  For this circuit we have

$I_1 + I_2 + I_3 = 0$ ,  $I_1 = g_{m1}(V_1 - 0)$ ,  $I_2 = g_{m2}(0 - V_2)$ ,  $I_3 = g_{m3}(0 - V_3)$  which yields

$$g_{m1}V_1 - g_{m2}V_2 - g_{m3}V_3 = 0 \text{ and } V_3 = \frac{g_{m1}V_1 - g_{m2}V_2}{g_{m3}}$$

5.21 We have  $V_3 = \frac{1}{sC}(I_1 + I_2)$ ,  $I_1 = g_{m1}(V_1 - 0)$ ,  $I_2 = g_{m2}(0 - V_2)$  which yields

$$V_3 = \frac{1}{sC}(g_{m1}V_1 - g_{m2}V_2)$$

5.22 The circuit realizes a NIC.

5.23 The transfer function for an inverting amplifier has been derive before

$$H(s) = -\frac{Z_2}{Z_1 + Z_2} = \frac{-\left(r_x + \frac{1}{sC}\right)}{Z_1 + \frac{1}{sC}} = \frac{-(s r_x C + 1)}{R - r_x + r_x + \frac{1}{sC}} = \frac{-(s r_x C + 1)}{(R - r_x) s C + \frac{sRC + 1}{A}}$$

For reasonable high frequencies we have  $A(s) = \omega_f/s$  where  $\omega_f = A_0 \omega_{3dB}$ . We get

$$H(s) = \frac{-(s r_x C + 1)}{(R - r_x) s C + \frac{(sRC + 1)s}{\omega_f}} = \frac{-(s r_x C + 1)\omega_f}{(sRC - r_x C \omega_f + \omega_f)RC + 1} s$$

We obtain, if we select  $r_x = \frac{1}{C\omega_f} = \frac{1}{10 \cdot 10^{-9} \cdot 10^5} = 1000 \Omega$ .

$$H(s) = \frac{-\left(\frac{s}{\omega_f} + 1\right)\omega_f}{(sRC - 1 + \omega_f RC + 1)s} = \frac{-(s + \omega_f)}{(s + \omega_f)RC_s} = \frac{-1}{RC_s} \text{ With this value of } r_x \text{ the real pole in the}$$

amplifier is cancelled. However, the pole must be known and remain constant, which is not the case in practice when, for example, the temperature varies. However, a significant improvement is obtained in practice.

5.24 The input impedance to the PI (gyrator) is found from

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 0 & r \\ V_2 \\ r & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \text{ and with}$$

$$Z_2 = 1/sC_2 \text{ we get } Z_{in} = \frac{r^2}{Z_2} = r^2 s C_2, \text{ i.e., the input impedance correspond to an inductor, with}$$

$$\text{inductance } L = r^2 C_2 = 6.75 \text{ mH. Hence, the transfer function is } H(s) = \frac{Z}{R+Z}$$

$$Z = \frac{sL \left( \frac{1}{sC_1} \right)}{sL + \frac{1}{sC_1}} = \frac{sL}{LC_1 s^2 + 1} \text{ and } H(s) = \frac{\frac{s}{RC_1}}{s^2 + \frac{s}{RC_1} + \frac{1}{LC_1}} \text{ i.e., a BP section. We get}$$

$$H(s) = \frac{\frac{s}{RC_1}}{s^2 + \frac{s}{RC_1} + \frac{1}{LC_1}} = \frac{10^4 s}{s^2 + 10^4 s + 1.481510^{10}} \text{ Hence, resonance frequency (pole radius) is } r_p = 1.2171 \cdot 10^5 \text{ rad/s and } Q = 12.1716.$$

5.25 a) With an ideal operational amplifier is the voltage between the inputs zero, i.e.,  $V_1 = V_2$ .

Denote the currents through the impedances from left to the right,  $I_1, I_2, I_3, I_4$  and  $-I_5$ .

$$Z_1 I_1 + Z_2 I_2 = 0 \Rightarrow I_2 = (-Z_1/Z_2) I_1$$

$$Z_3 I_3 + Z_4 I_4 = 0 \Rightarrow I_4 = (-Z_3/Z_4) I_3$$

$$V_2 = -Z_5 I_5 \Rightarrow V_2 = -Z_5 I_5 = -Z_5 (Z_3/Z_4) I_3 = -Z_5 (Z_3/Z_4) (-Z_1/Z_2) I_1$$

$$I_2 = I_3$$


$$I_4 = -I_5$$

$$V_1 = V_2 \text{ and finally } Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

b) We have from above  $V_1 = V_2$  and  $I_1 = (-Z_2/Z_1) I_2 = (-Z_2/Z_1) I_3 = (-Z_2/Z_1) I_5 (Z_3/Z_4)$  and finally  $I = (Z_2 Z_4 / Z_1) I_5 (-I_5)$  where  $I_5$  is the current into port 2. Comparing with the definition for the  $\mathbb{K}$  matrix yields

$$\mathbf{K} = \begin{bmatrix} 1 & 0 \\ 0 & \frac{Z_2 Z_4}{Z_1 Z_3} \\ 0 & \frac{Z_2 Z_4}{Z_1 Z_3} \end{bmatrix}$$

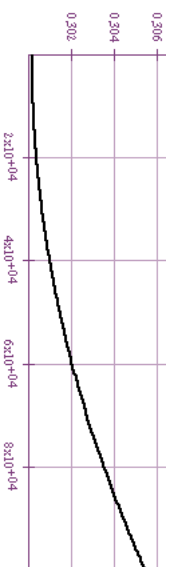5.26 a) Select relatively small resistors, e.g.,  $R_2 = R_3 = 10 \text{ k}\Omega$  in order to obtain low sensitivity for parasitic stray capacitances. Select, e.g.,  $C_4 = 10 \text{ nF}$  which yields  $sL = Z_1 s^2 C_4 Z_5$  and select, e.g.,  $R_1 = R_5 = 5.48 \text{ k}\Omega$ . With an operational amplifier with  $\omega_T = 20\pi \text{ Mrads}$  we get the inductance (magnitude of  $Z_{in}/j\omega$ ) according to the figure below.



b) Select, e.g.,  $R_4 = R_5 = 10 \text{ k}\Omega$  and  $C_1 = C_3 = 330 \text{ nF}$  which yields  $R_2 = \frac{D}{C_1 C_3} = 91.83 \text{ k}\Omega$ .

5.27 We have  $Z_1 = \frac{1}{sC_1}$   $Z_2 = R_2$   $Z_3 = \frac{R_3}{1+sR_3C_2}$   $Z_4 = R_4$   $Z_5 = R_5$

We have for an ideal operational amplifier, i.e.,  $V_+ = V_-$

$$V_{in} = R_1 I_{in} - R_5 I_5 \Rightarrow I_5 = (R_1 I_{in} - V_{in})/R_5$$

$$Z_1 I_{in} + Z_2 I_2 = 0 \Rightarrow I_{in} = -Z_2 I_2 / Z_1 \Rightarrow I_{in} = (-Z_2 Z_1) (Z_4 / Z_3) I_5$$

$$Z_3 I_2 - Z_4 I_5 = 0 \Rightarrow I_2 = Z_4 I_5 / Z_3$$

$$V_2 = -(R_4 + R_5) I_5 \Rightarrow V_2 = -(R_4 + R_5) I_5$$

$$\text{which after simplification we get } \frac{V_2}{V_{in}} = \frac{(Z_4 + Z_5) Z_3 Z_1}{R_1 Z_2 Z_4 + Z_1 Z_3 Z_5}$$

With  $R_1 = R_2 = R_4 = R_5 = R$ ,  $R_3 = Q R$  and  $C_1 = C_2 = C$  and  $r_p = 1/RC$  we get the transfer function according Eq.(9.4), i.e., an LP section. Select, e.g.,  $C = 10 \text{ nF}$  and  $R = 1/(r_p C) = 5.0 \text{ k}\Omega$  and  $R_3 = Q R = 1/\sqrt{2} = 3.5255 \text{ k}\Omega$ . The section DC gain is 2. The gain can be reduced by replacing  $R_1$  with a voltage divider. If  $R_1$  is split into two equal size resistors with the resistance  $2R_1$ , the section DC gain = 1.