

4.17 $S = \frac{Z - R}{Z + R}$ where $Z = jX$ for a reactance. Hence,

$$S = \frac{jX - R}{jX + R} = \frac{(jX - R)(-jX + R)}{(jX + R)(-jX + R)} = 1$$