

5.4 For a two-port adaptor we have

$$\begin{aligned}b_1 &= a_2 + \alpha(a_2 - a_1) \\b_2 &= a_1 + \alpha(a_2 - a_1) \\ \alpha &= \frac{R_1 - R_2}{R_1 + R_2}\end{aligned}$$

The pseudo-power entering into the adaptor is

$$p = \frac{1}{R_1} (a_1^2 - b_1^2) + \frac{1}{R_2} (a_2^2 - b_2^2)$$

Simple, but long and tedious simplification, yields $p = 0$.